

Automatic Control

Hak-Tae Lee


Dynamics

Models of Electric Circuit

Models of Electric Circuit





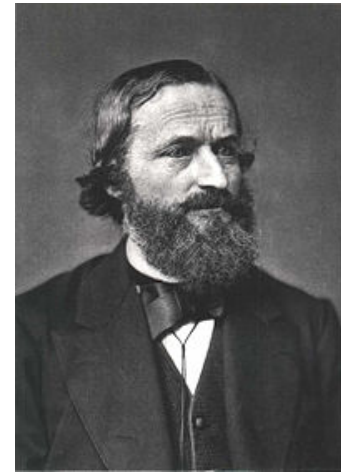


- Electric circuits
 - Interconnections between sources of electric voltage and current, and other electric elements
 - 3 passive elements: resistor (R), inductor (L), capacitor (C)
 - Other elements:
 - Operational amplifiers
 - Transistors
- Why?
 - Actual implementation of control system is in the form of electric circuits

Kirchhoff's laws



- Kirchhoff
 - Gustav Robert Kirchhoff (1824 – 1887), German physicist
 - Electric circuits, spectroscopy, black-body radiation
- Kirchhoff's laws
 - KCL (Kirchhoff's Current Law): The algebraic sum of currents leaving a junction or node equals the algebraic sum of the currents entering that node
 - KVL (Kirchhoff's Voltage Law): The algebraic sum of all voltages taken around a closed path in a circuit is zero

Elements of Electric Circuits

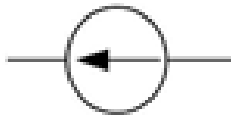
Circuit Element	Symbol	Schematic
Resistor	R	 or 
Inductor	L	
Capacitor	C	
DC Voltage Source	V_s	 or 
DC Current Source	I_s	

$$v = iR$$


$$v = L \frac{di}{dt}$$

$$i = C \frac{dv}{dt}$$


Ohm's Law

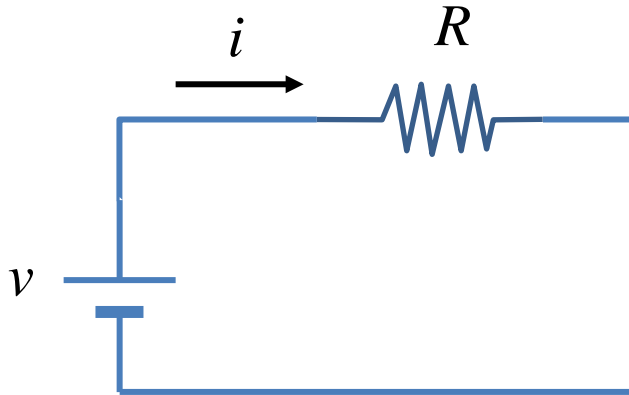

$$i = \frac{v}{R}$$

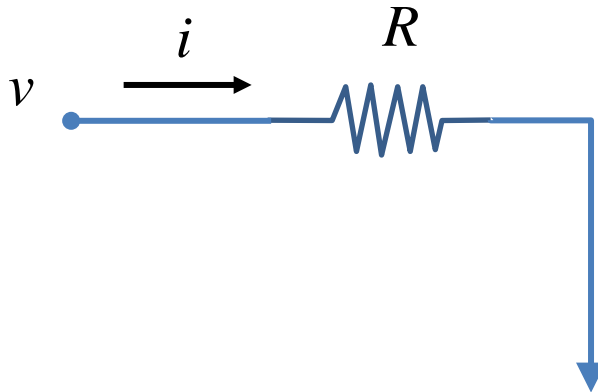


Ohm's Law

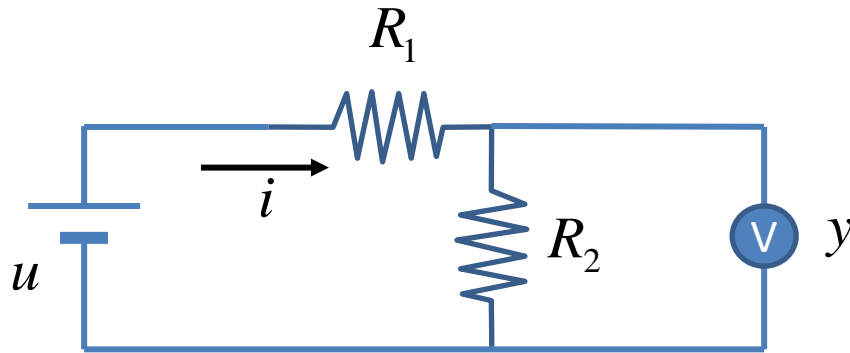



$$i = \frac{u}{R_1 + R_2}$$

$$y = iR_2$$

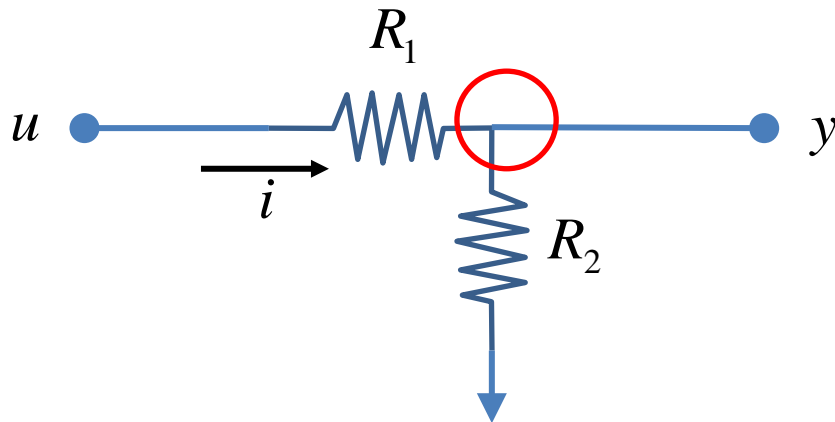

$$\frac{u - y}{R_1} = \frac{y - 0}{R_2}$$

Circuits with Capacitors

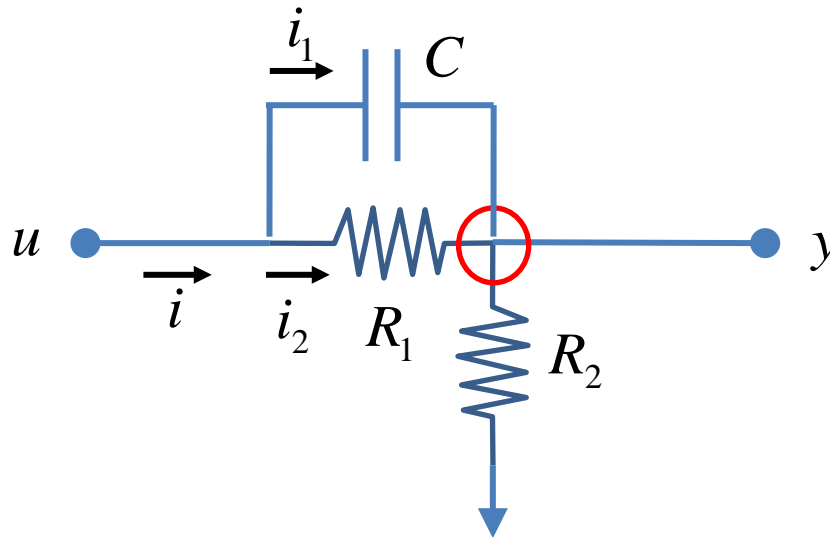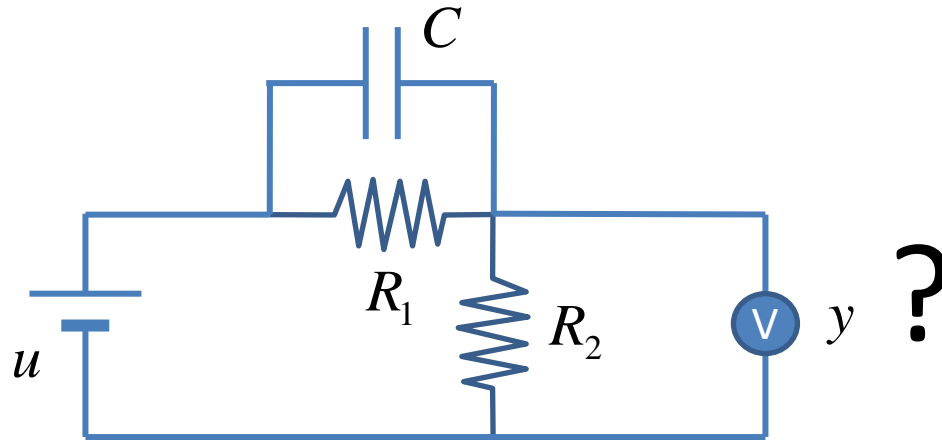


$$\text{KCL: } i = i_1 + i_2$$

$$i_1 = C \frac{d(u - y)}{dt} \quad i_2 = \frac{(u - y)}{R_1}$$

$$i = \frac{(y - 0)}{R_2}$$


$$C\dot{u} + \frac{1}{R_1}u = C\dot{y} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right)y$$

Circuits with Capacitors

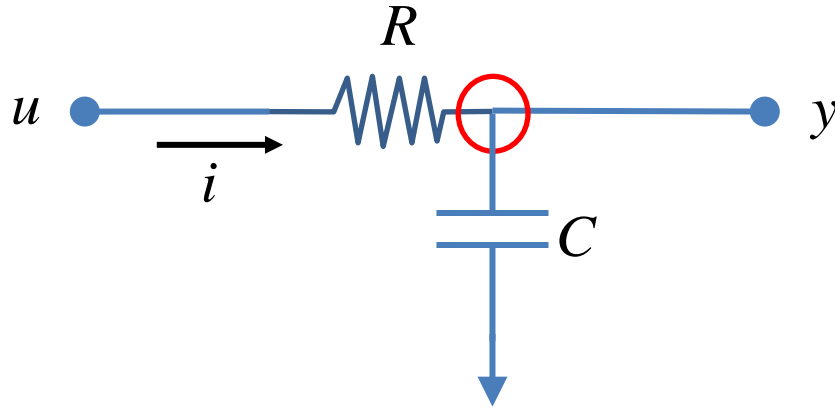


$$\frac{u - y}{R} = C \frac{d(y - 0)}{dt}$$


$$y + RC\dot{y} = u$$

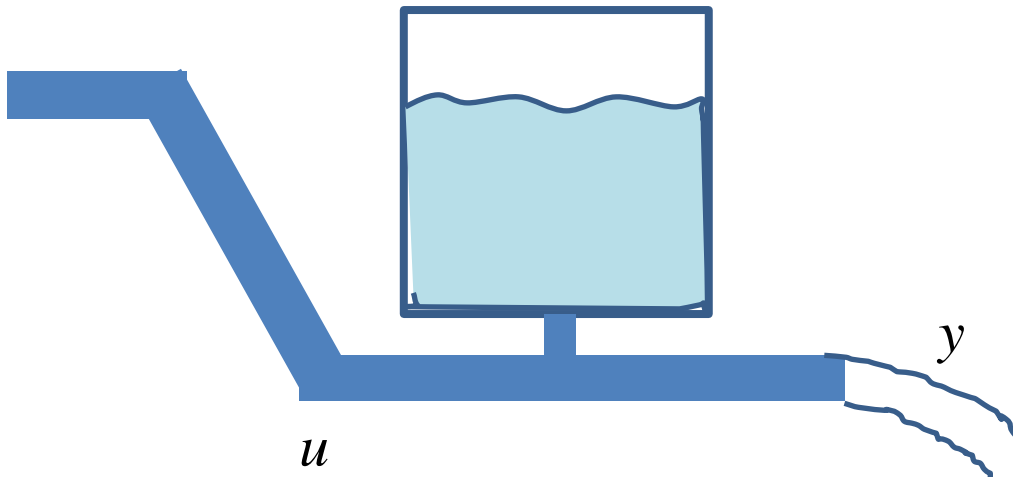


Response – Small Capacitance

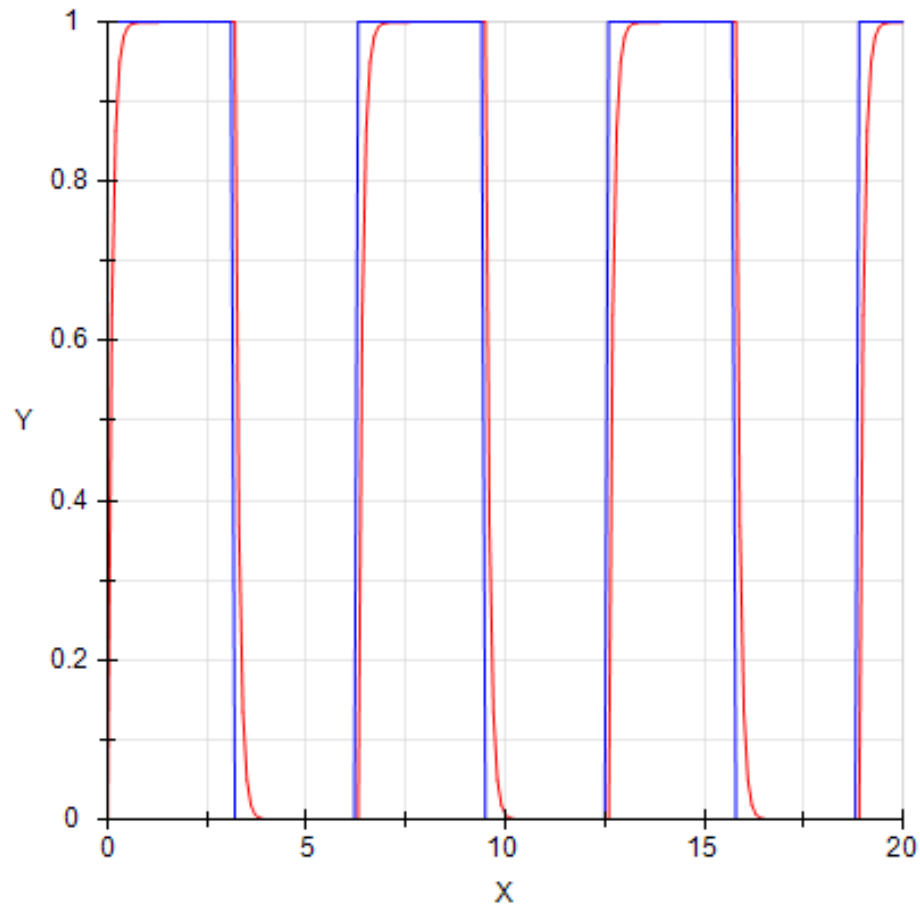

Response – Large Capacitance

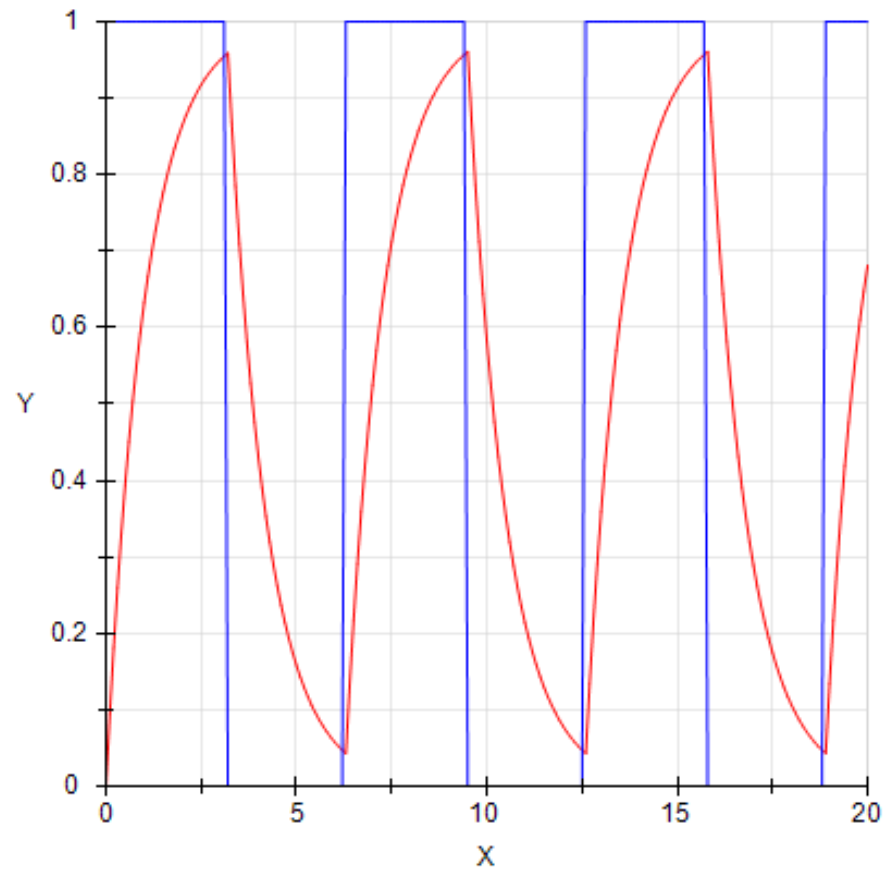

RLC Circuit

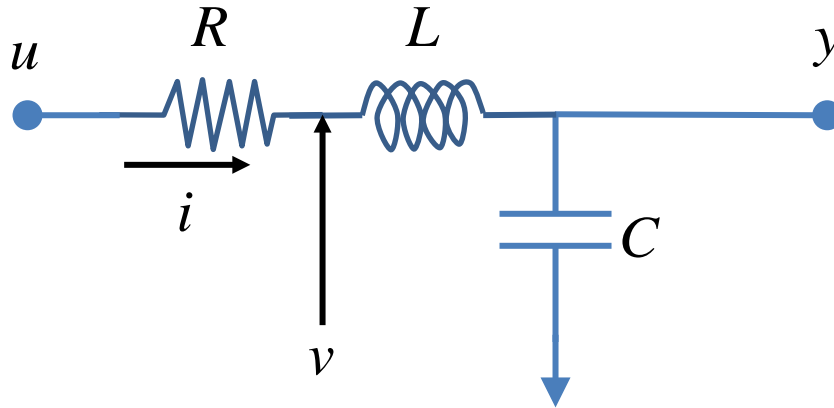

$$i = \frac{u - v}{R}$$

$$L \frac{di}{dt} = (v - y)$$

$$C \frac{dy}{dt} = i$$


$$LC\ddot{y} + RC\dot{y} + y = u$$

Compare this with

$$m\ddot{y} + b\dot{y} + ky = u$$

Operational Amplifier

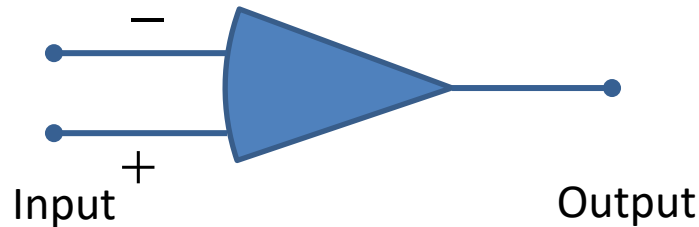- DC-coupled high-gain voltage amplifier with a differential input and a single output
- Building blocks for analogue circuit design





Operational Amplifier

- Text book description
 - Output voltage = (Large gain) x (voltage difference between the two inputs)
- What it actually does
 - OP Amp make sense only in a constructed circuit
 - It adjust the output voltage until the two input voltage becomes the same
 - No current flows in/out through the inputs



OP Amp Circuits

Inverting amplifier

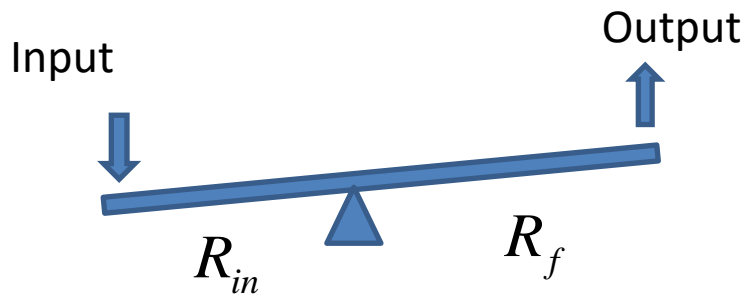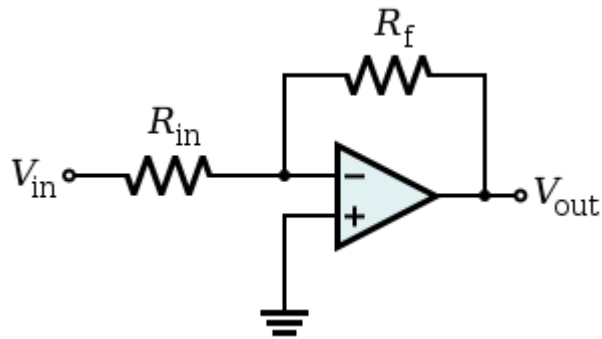

$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$


Non-inverting amplifier

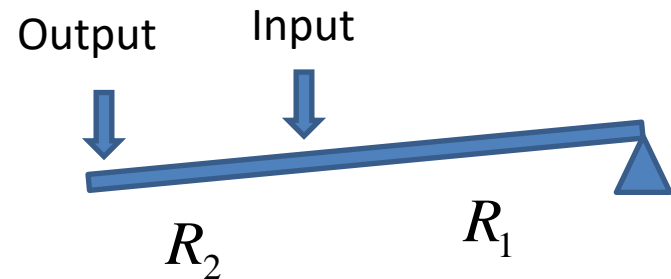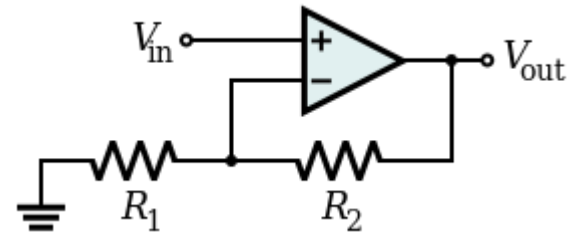

$$V_{out} = \frac{R_1 + R_2}{R_1} V_{in}$$


OP Amp Circuits

Voltage follower (unity buffer)

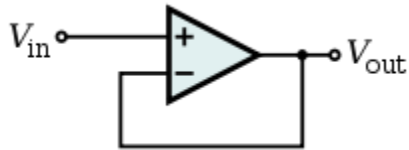

$$V_{out} = V_{in}$$

Summing amplifier

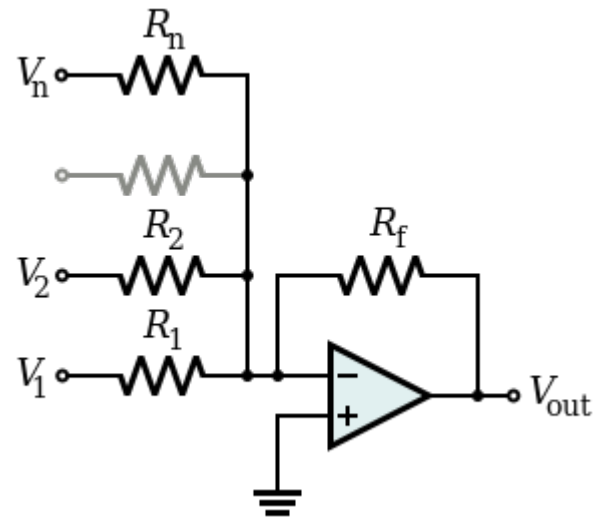


$$V_{out} = -R_f \left(\frac{1}{R_1} V_1 + \frac{1}{R_2} V_2 + \dots + \frac{1}{R_n} V_n \right)$$




Integrator and Differentiator

Inverting integrator

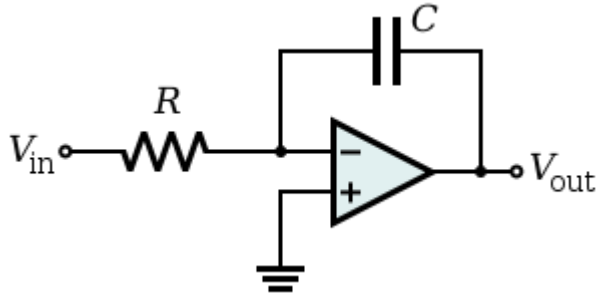


$$V_{out}(t_1) = V_{out}(t_0) - \frac{1}{RC} \int_{t_0}^{t_1} V_{in}(t) dt$$

Inverting differentiator

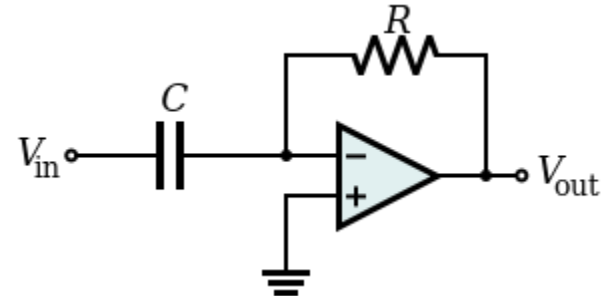

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Exercise 1

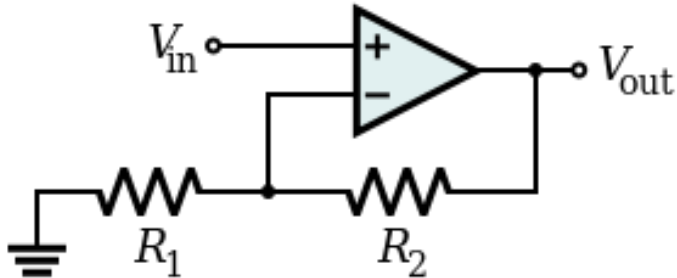

Your pressure sensor's output voltage ranges from 0 to 0.5 V for the pressures that you want to measure.

Your A/D converter is 5 V. Pick your resistor values so that the non-inverting amplifier scales the sensor output voltage to fit the A/D converter input voltage.

Exercise 2

To make a PD controller, you need to generate a signal u that is linear combination of input signal e and its derivative.

Construct an op-amp circuit to perform this.

$$u = ae + b\dot{e}$$